

Physics

Chapter 15

Galvanometer

"It is a basic electro mechanical instrument used to detect and measure small amounts of currents"


- i) Moving Coil Galvanometer
- ii) Moving Magnetic Galvanometer

Principle :-

It is based on the interaction between a current and magnet when a current flows in a

rectangle coil placed in a magnetic field. It experiences a magnetic torque and rotates. Thus electrical energy is converted into mechanical energy.

Construction

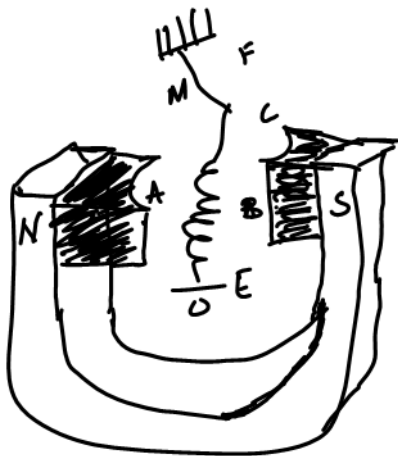

The moving coil galvanometer consists of a U-shaped magnet with a coil suspended between its poles. The insulated copper wire is wound over a non-magnetic ~~of~~ material (C). The first current lead is (A) and second current lead is (E).

Working :-

When current (i) is passed through the coil, the coil is acted upon by deflecting couple

which tends to rotate the coil. The deflecting couple is the deflecting torque,

$$\text{Deflecting torque} = BIAN \cos \alpha$$

The coil while turning will twist the suspension wire.

As a result opposing torque is developed called the restoring torque, ~~the~~ whose magnitude is equal to the ~~the~~ twist in the suspension. (9)

Restoring torque $\propto \theta$

$$\text{Restoring torque} = C\theta$$

Where C is called couple per unit twist (for suspension)

In Equilibrium Condition

$$\text{Deflecting Torque} = \text{Restoring Torque}$$

$$B \sin \alpha \cos \alpha = C\theta$$

$$I = \frac{C\theta}{B \sin \alpha \cos \alpha}$$

$$\checkmark \quad I = \left(\frac{C}{BAN} \right) \theta$$

$$I = \text{Constant} \times \theta$$

$$I \propto \theta$$

Sensitivity of Galvanometer ~

Galvanometer is said to be more sensitive if it gives a large deflection with the same value of current.

$$\text{Sensitivity} = \frac{\text{Deflection}}{\text{Micro ampere current}}$$

$$\text{Sensitivity} = \frac{\theta}{I} \quad - (1)$$

$$\frac{1}{C/BAN} = \frac{\theta}{I} \quad - (2)$$

By comparing

$$\text{Sensitivity} = \frac{C}{BAN}$$


Ammeter :-

An electrical instrument which is used to measure current passing through a circuit.

Principle

It works on the same principle as moving coil galvanometer.

Construction

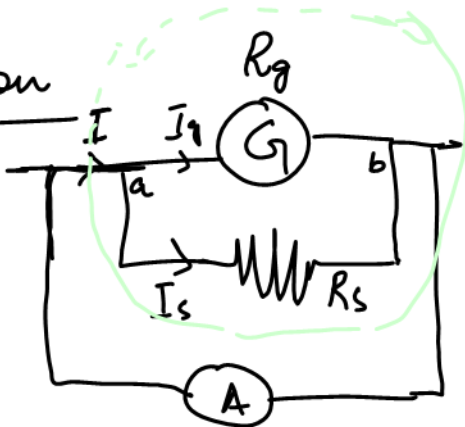

To convert a galvanometer into an ammeter a small resistance (R_s) is connected parallel to galvanometer. This resistance is called shunt resistance.

Calculation of (R_s):-

Let (I_g) be the current in galvanometer which gives full scale deflection, due to its resistance (R_g).

$$\text{So, } V_g = I_g R_g$$

But, when we connect a
a shunt resistance, the current
(I) is divided at the terminal
a into (I_g) and (I_s)

$$I = I_g + I_s$$

$$I_s = I - I_g$$

where (I_s) is current passing
through shunt. Then,

$$V_s = I_s R_s$$

Since in parallel

$$V_s = V_g$$

$$\begin{aligned} \bar{I}_s R_s &= \bar{I}_g R_g \\ \rightarrow R_s &= \frac{\bar{I}_g R_g}{\bar{I}_s} \end{aligned}$$

$$R_s = \frac{\bar{I}_g R_g}{I - \bar{I}_g}$$



